

ENGR 210 / CSCI B441  
“Digital Design”

# SPI II

Andrew Lukefahr

# Announcements

- P8 – Elevator Controller is out

- This one is hard.

due Friday

- P9 – SPI is out

→ Last one 😊

- This one is new. Might be some changes.

- The end is in sight...

# P9 SPI QuickStart

- We build the Vivado project for you:

```
git clone https://github.com/ENGR210/P9\_SPI.git  
cd P9_SPI  
make setup  
vivado vivado/vivado.xpr
```


- We provide you with Testbenches
- Same ones as the Autograder!

Always specify  
defaults for  
**always\_comb!**


**BLOCKING (=) FOR**  
**always\_comb**

**NON-BLOCKING (<=) for**  
**always\_ff**


# Glitch

 

 Results in a short low-going pulse at the output of  $N_2$  with length approximately equal to the propagation delay through  $N_1$ .




# Setup/Hold Time

 
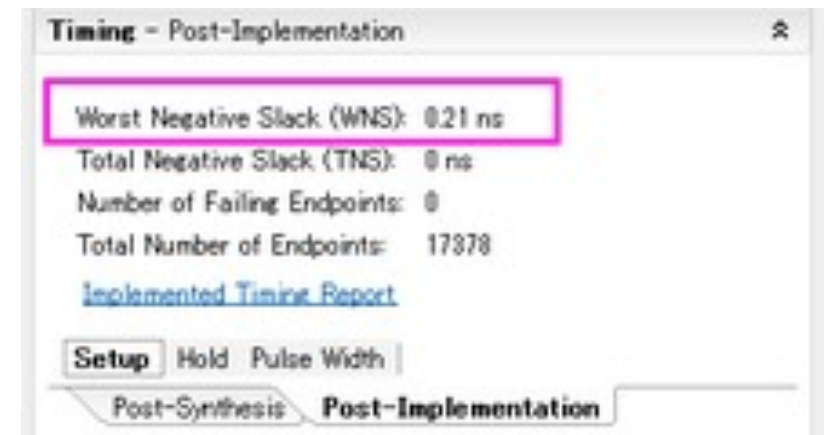
# Slack

- Extra time between combinational propagation delay and setup time
- Time between stable input to Flip-Flop and next clock edge

- Vivado:
  - WNS: Worst-case Negative Slack



- If this number is  $<0$ , your circuit will (probably) not work



# Correct for ( ; ; ) Loops in Verilog

## This Code:



```
integer x; //or genvar x
for (x = 0; x < 4; x++) begin
    assign y[x] = a[x+right];
end
```

## Expands to:


```
assign y[0] = a[0 + right];
assign y[1] = a[1 + right];
assign y[2] = a[2 + right];
assign y[3] = a[3 + right];
```

Converts serial input to parallel output

# Shift Register

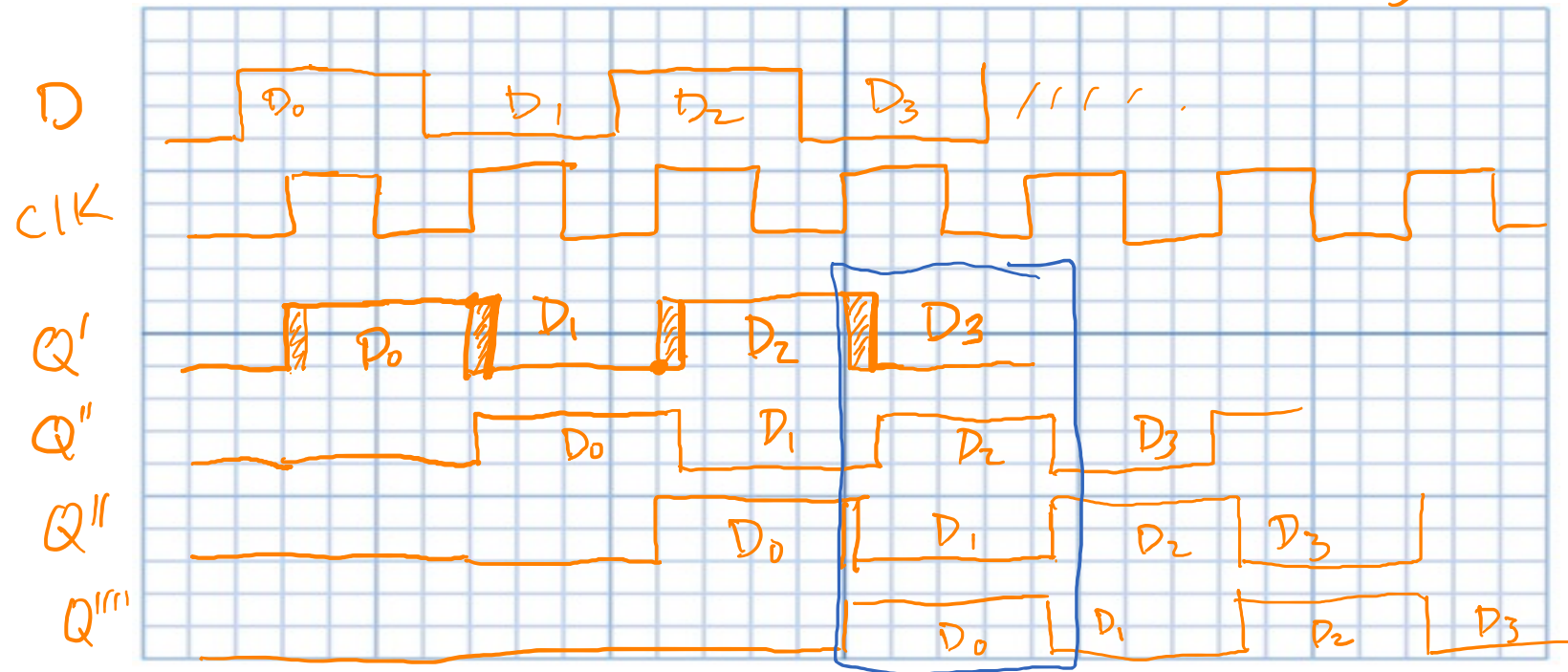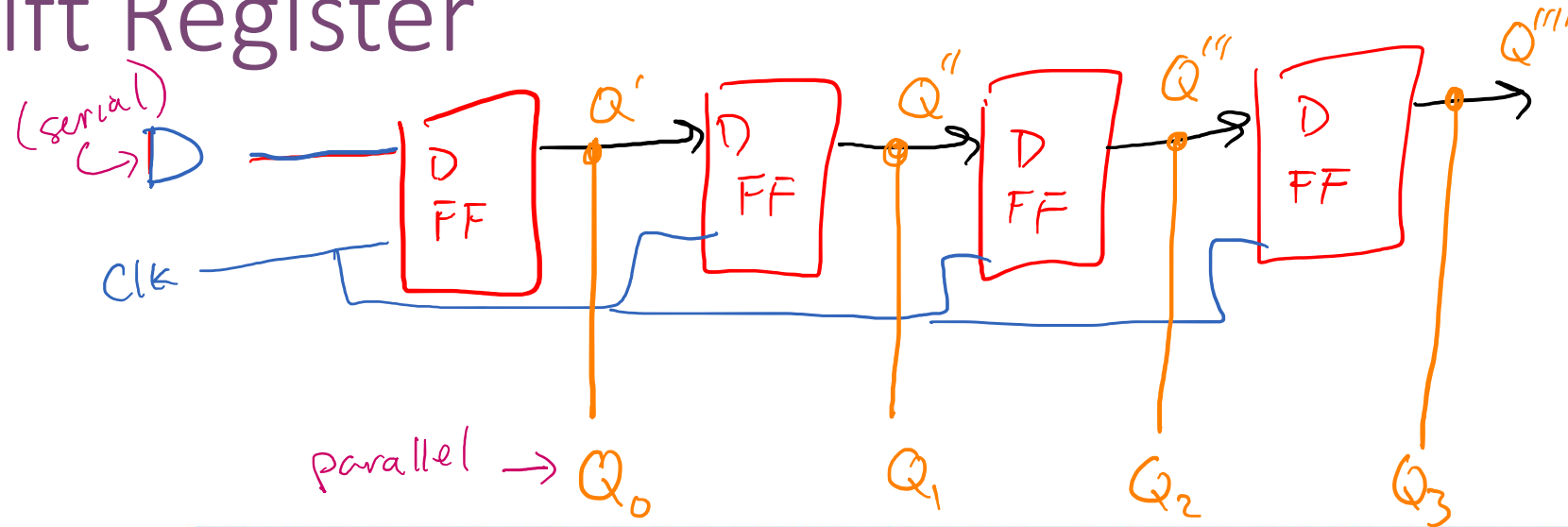


What about this circuit?

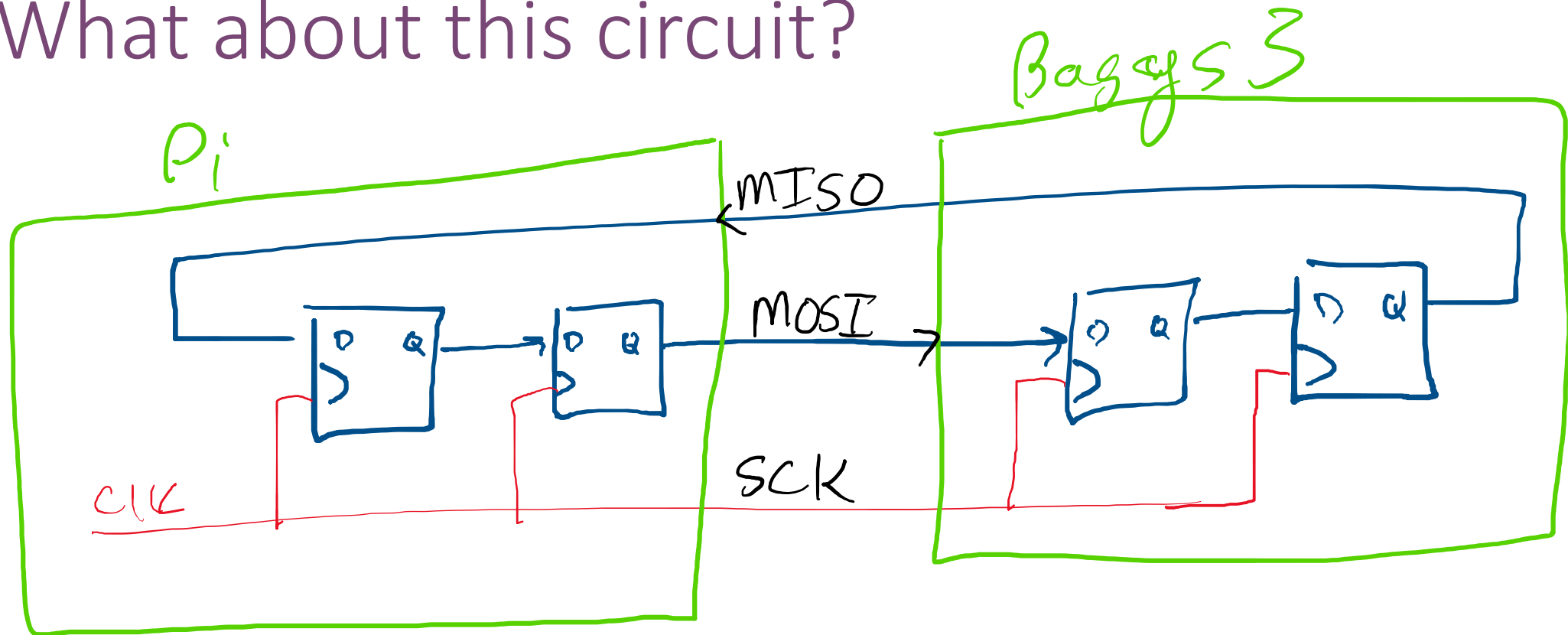

MOSI: Master Out Slave In  
Serial Data out (SDO)

MISO: Master In Slave Out  
Serial Data In (SDI)


# SPI

 

# When to CAPTURE new data?



Rising Edge of SCK!

 

# When to SEND new data?




Ⓞ falling  
SCK



edge of

~~CLOCK~~  
SCK



~~DATA~~  
MISO

 

# Clocks on Slave SPI

 
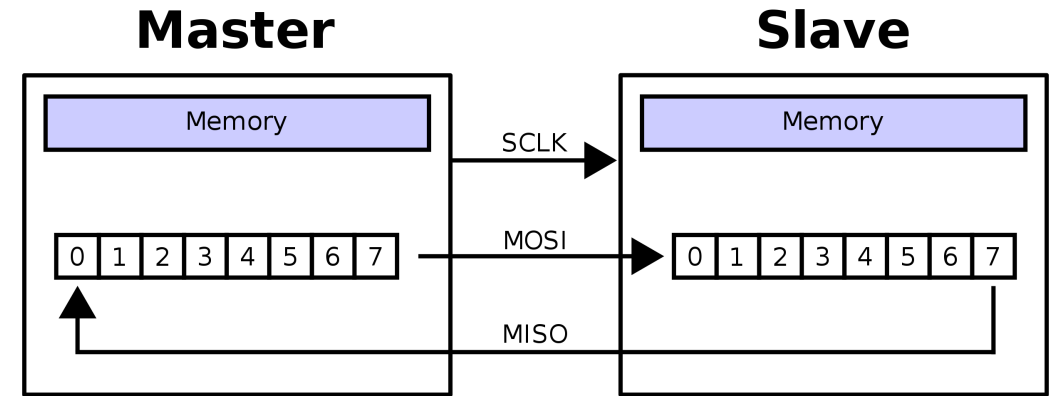


# Clocks on Slave SPI

  





# Clocks on Slave SPI

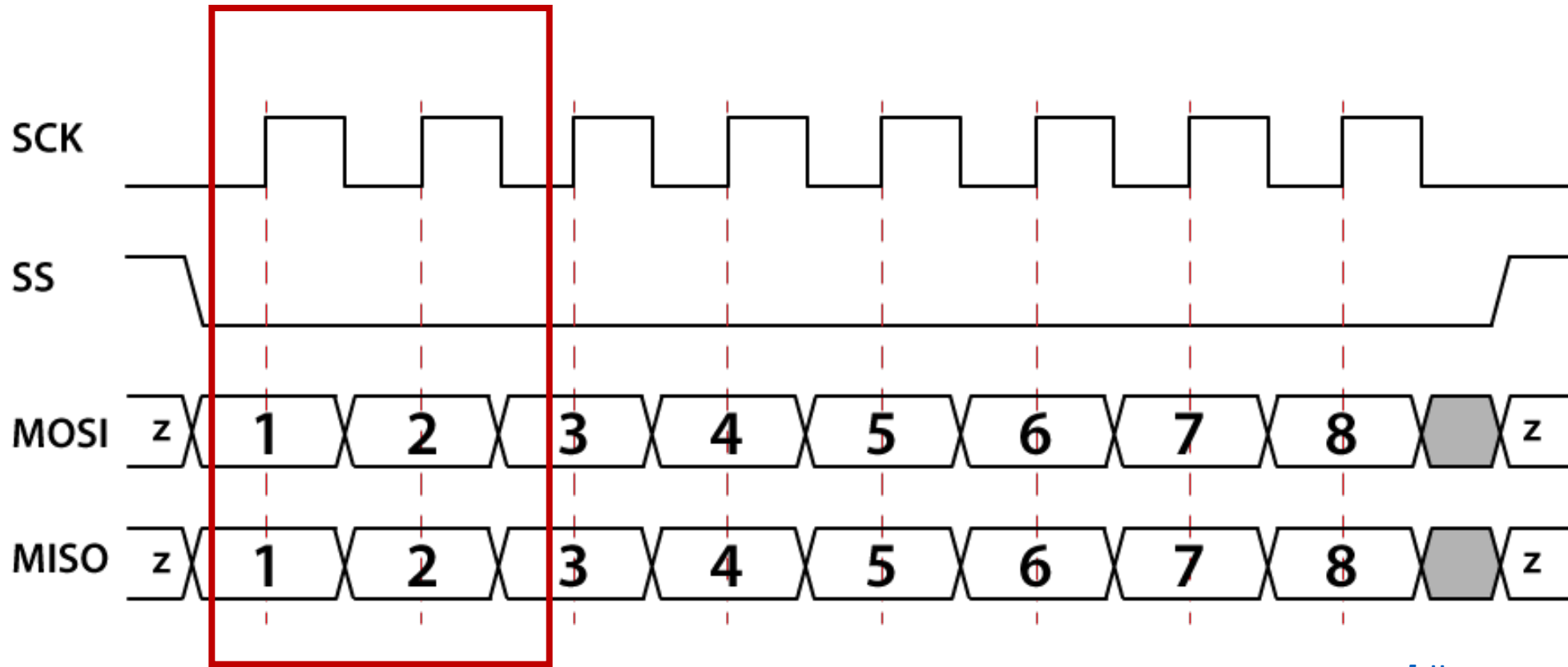 


# Clocks on Slave SPI

 


CLK100MHz

 

# Finding SCLK Edges

 


# Finding SCLK Edges

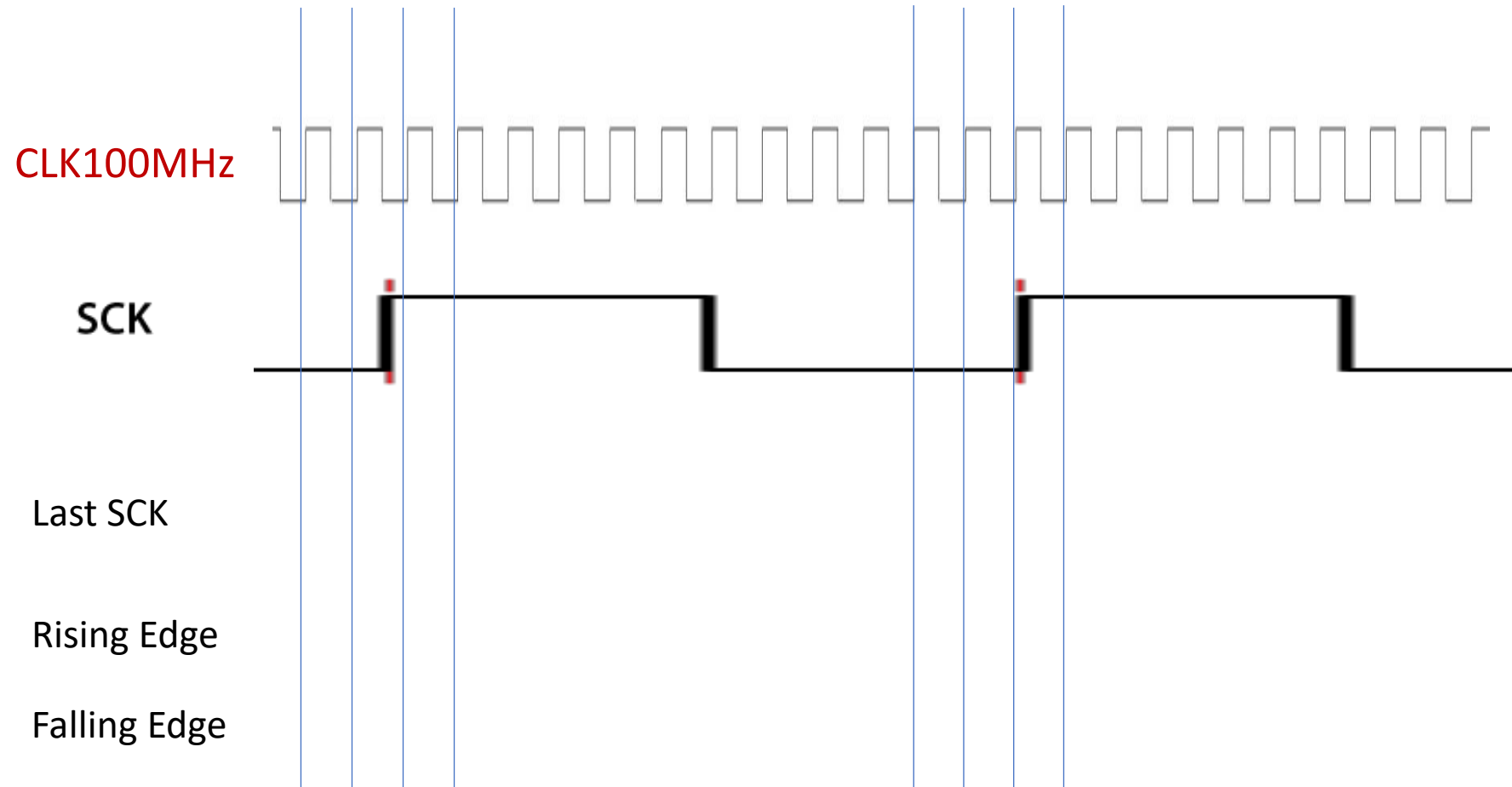


# How to capture MOSI?

Not 100% right yet!

 


# When to send MISO?

 


# How to send MISO?

Not 100% right yet!

 


# Timing Issues?

 




# Timing Issues

 

# Setup/Hold Time


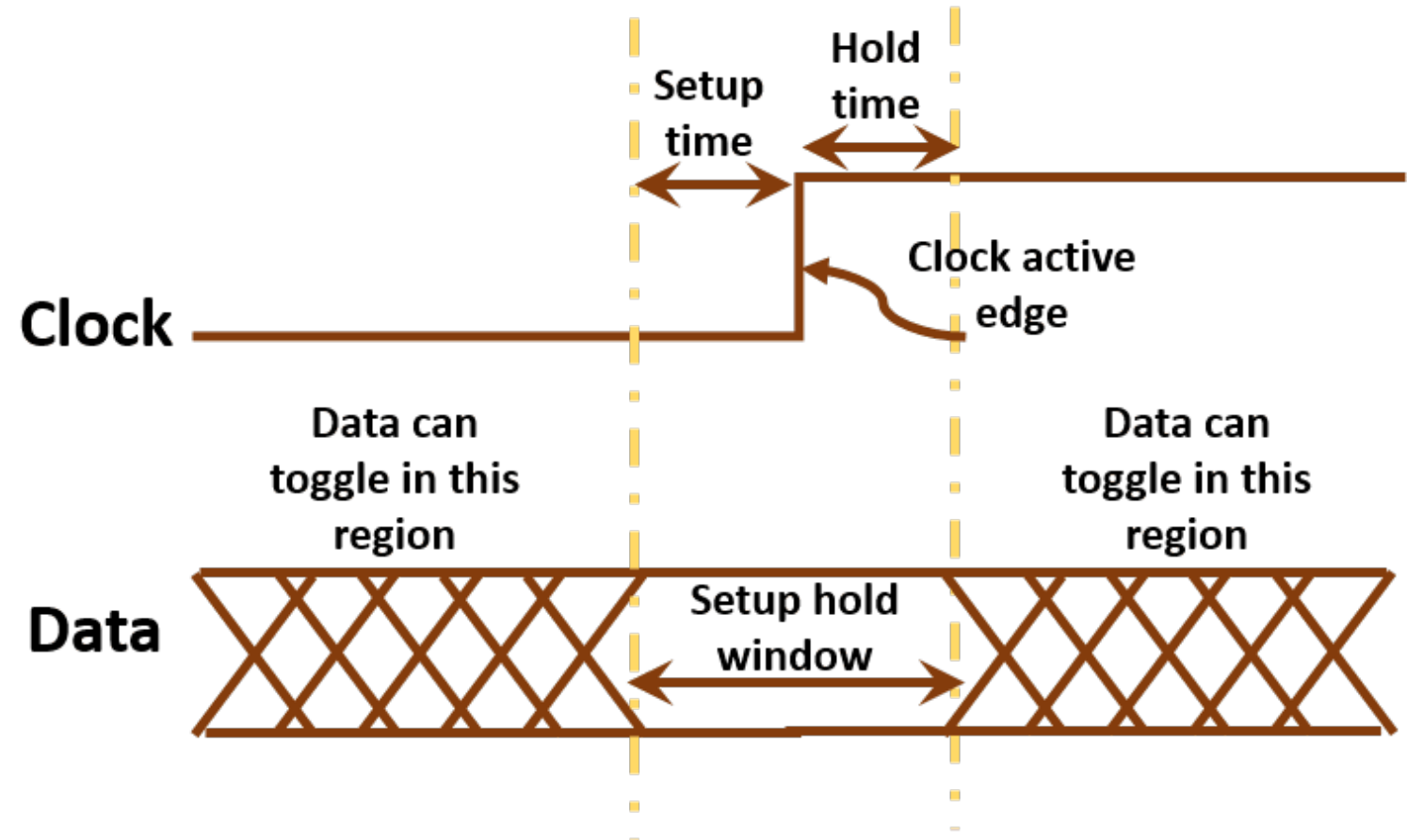


# Next Time

- Synchronizers
- Tri-State Logic
- MMIO



# Why Synchronizers?

# Synchronizers

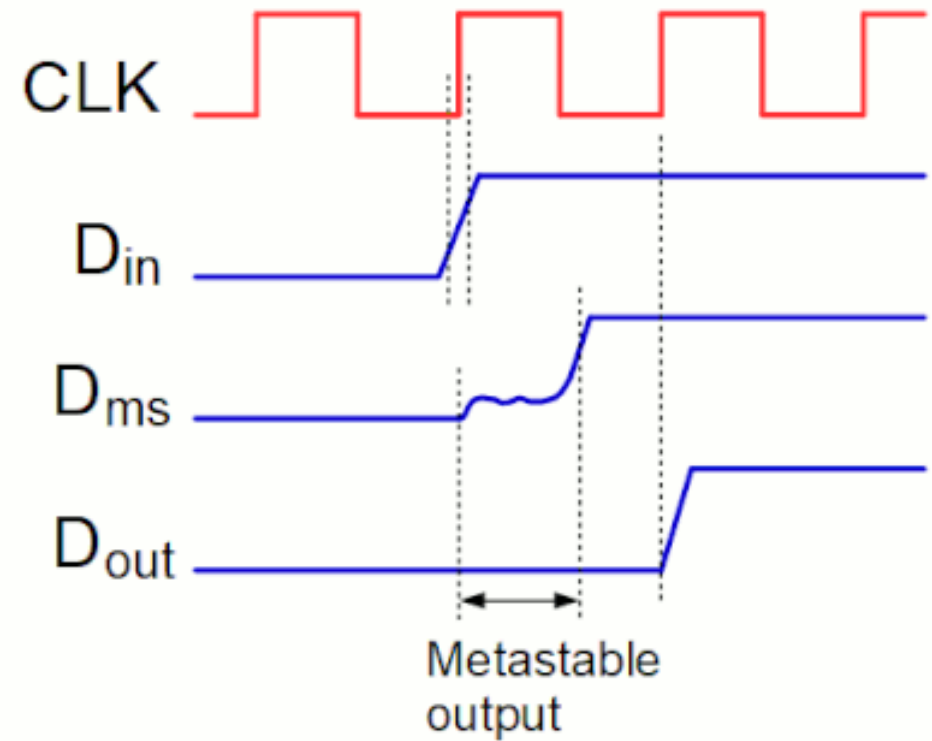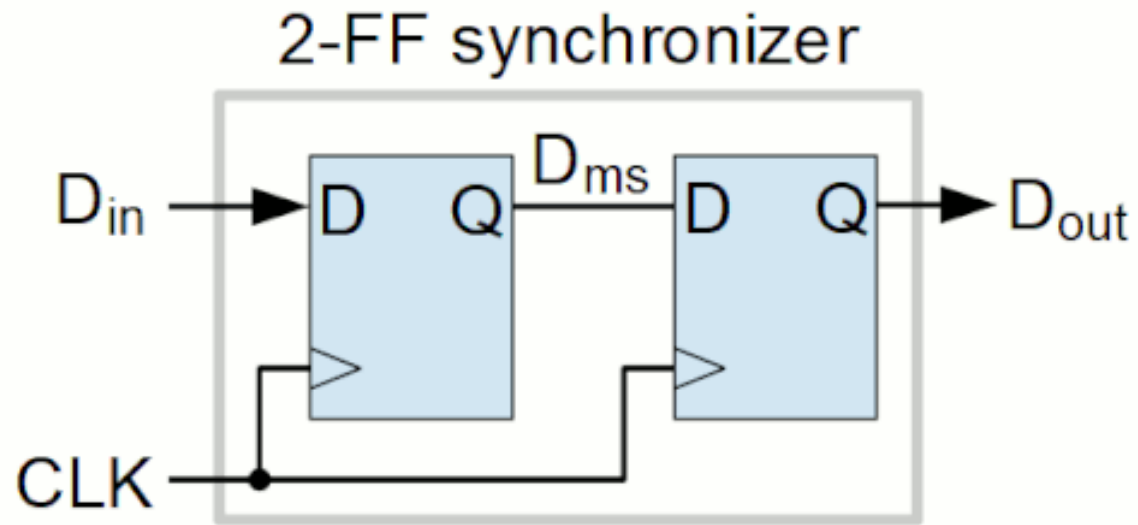



# What about 'Z'?

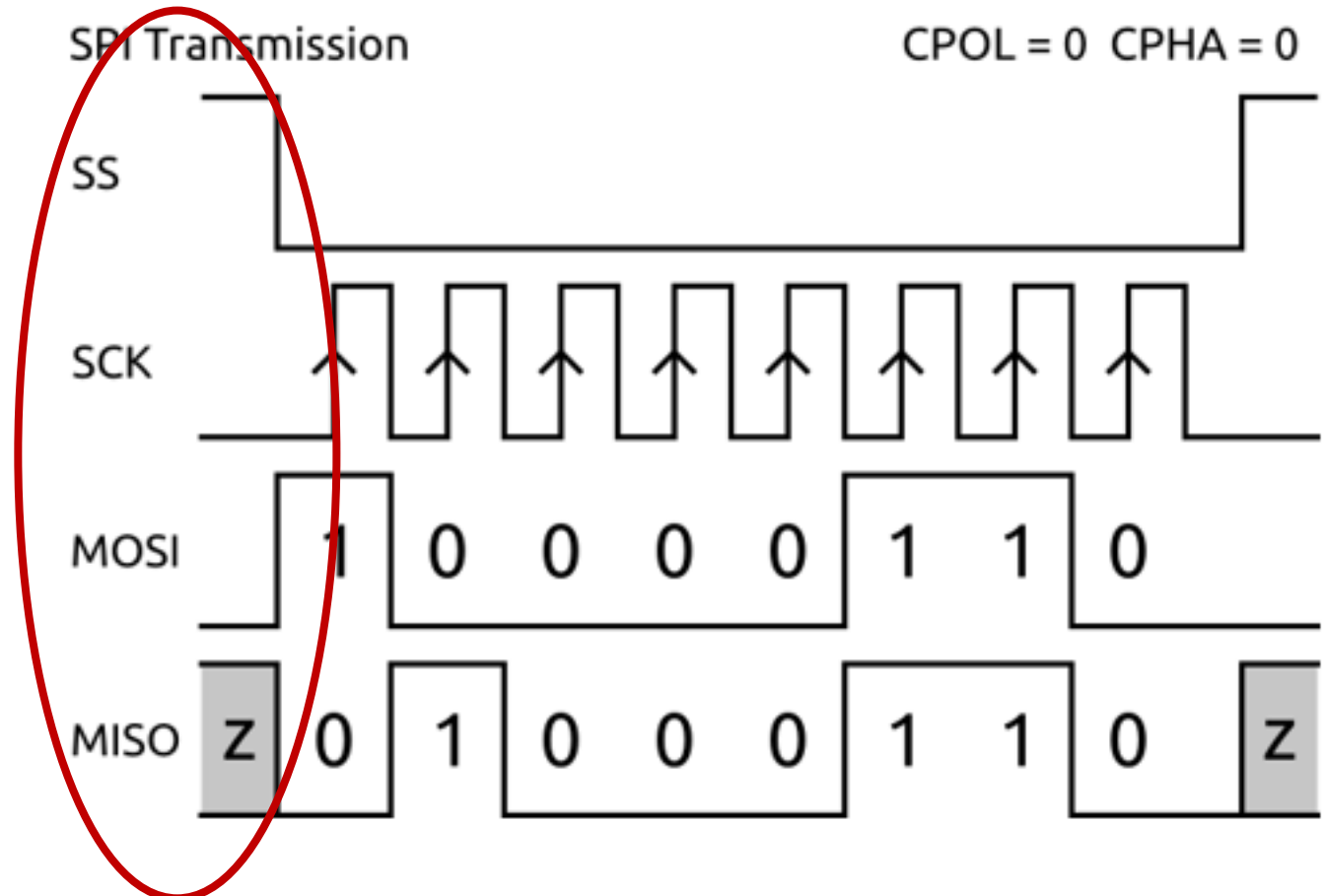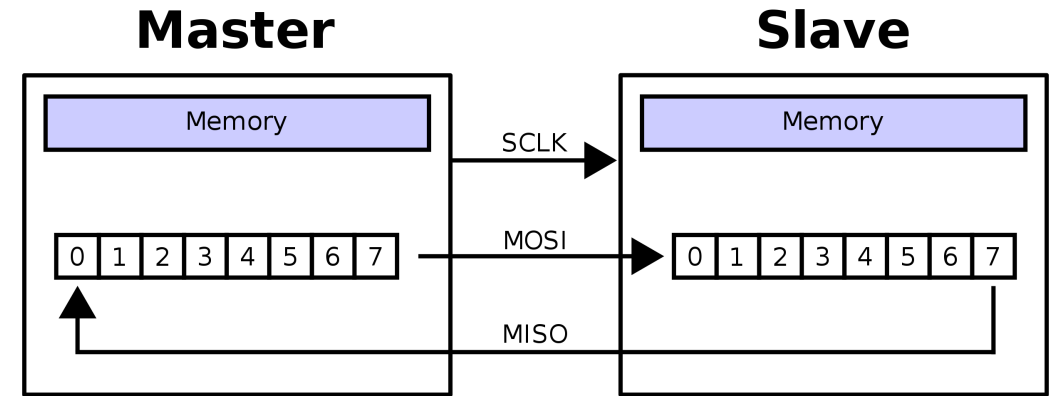

# What is 'Z'?


- Z: High Impedance
  - Stop driving a logical value
  - Pretend I'm not connected
- “Tri-State” signals:
  - 1: this is logical true
  - 0: this is logical false
  - X: The simulation tools don't know if it's 1 or 0
  - Z: this is “high impedance”



# Tri-State Logic

# Problems with Tri-State Logic

- What if two signals “drive” at once?

 

Solution: Don't Do That!

**NEVER DO THAT!**